
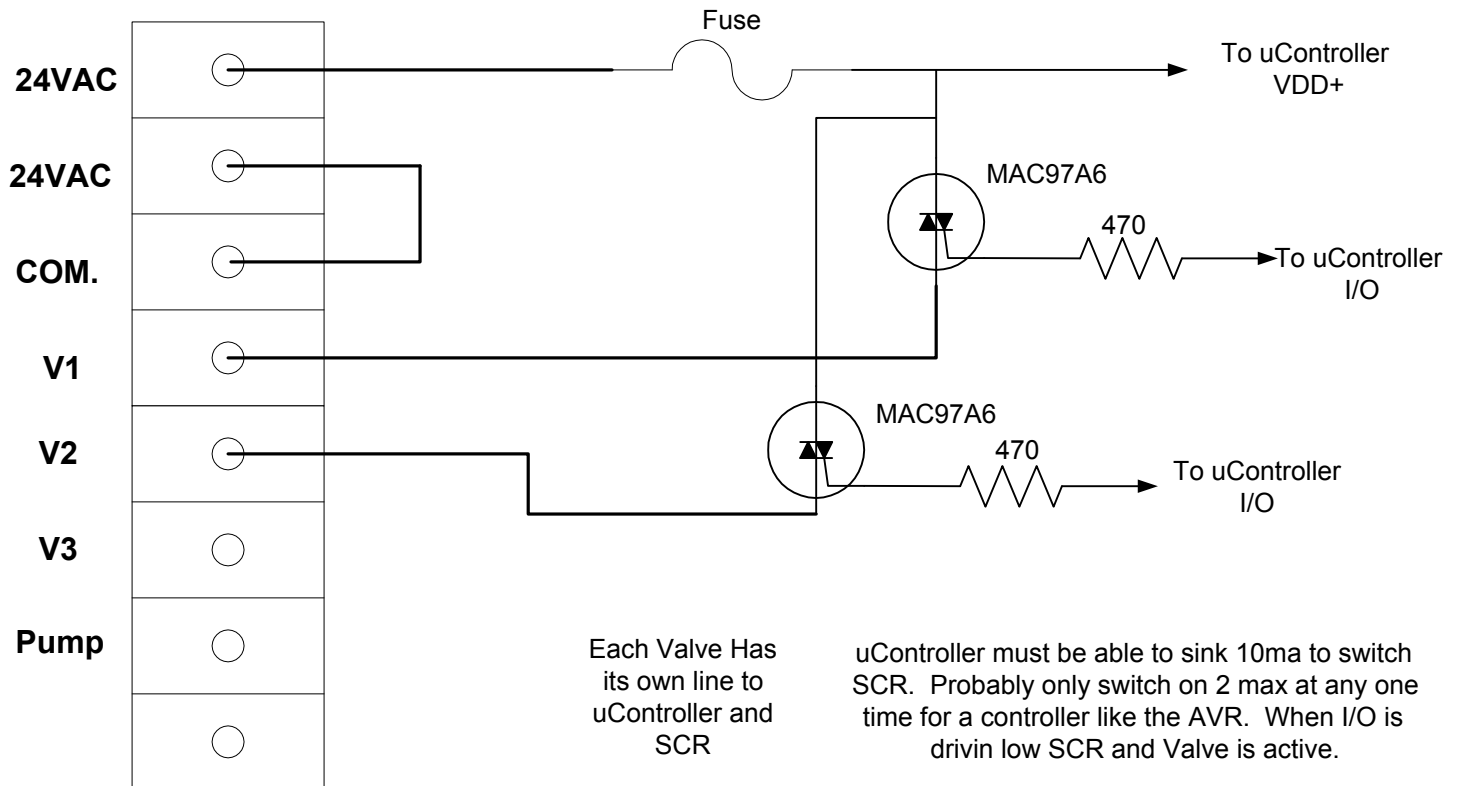
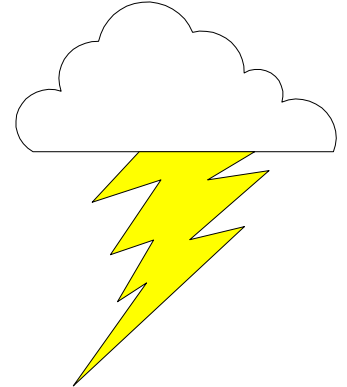
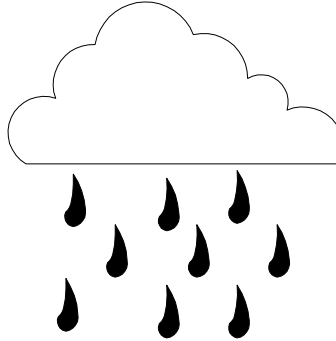
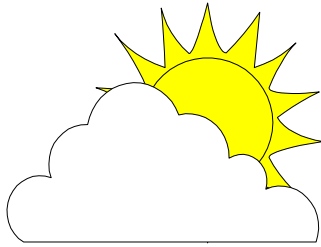


Irrigation Valve Control

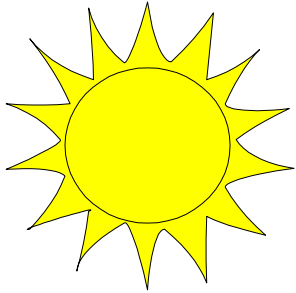from a uController (c)2000 mycal labs www.mycal.net



This design can control higher voltages than 24VAC, but I recommend using a photo SCR to switch dangerous voltages and current.