
Power Meter/Dummy Load

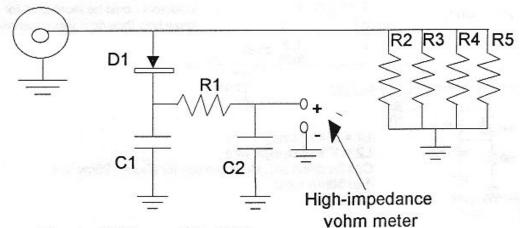

D1 - 1n4148

R1 - 22K

C1 - 47pf

R2, R3, R4, R5 - 200 ohm 1/2 watt

C2 - .1uf

Note: R2, R3, R4 and R5 could be 1/4 watt for a maximum power handling of about 1 watt, as shown it can hadle 2 watt. The resistors could be replaced with 1 watt or 2 watt carbons for even more power handling ability. Do not use wirewound resistors! You can use the device shown for up to 6 watts of short term testing, just watch the temp!

To calculate power output use the formula:

Power Output =
$$E^2 / 50$$


Example if you mesue 2 volts on your VOM:

Power Output =
$$\frac{2}{2}/50$$

= 4/50
= .08 watts
= 80 mw

volts	power
2v	80mw
3v	180mw
4v	320mw
5v	500mw
6v	720mw
7v	980mv

PART PLACEMENT

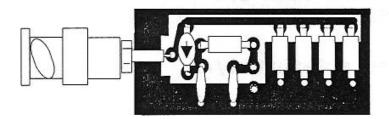

PCB BOARD (actual size)

